

STEM DESIGN CHALLENGE

Using 1 bulb, 1 battery and 1 switch, create a bedside paper lamp.

Draw the lamp below. Where will you put the light? Build your circuit. Secure the connections with tape.

